

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

MULTIMEDIA UNIVERSITY

SUPPLEMENTARY EXAMINATION

TRIMESTER 1, 2015/2016

EEL1166 – CIRCUIT THEORY
(All sections / Groups)

17 NOV 2015
9.00 AM – 11.00 AM
(2 HOURS)

INSTRUCTIONS TO STUDENTS

1. This Question paper consists of 6 pages with 4 Questions only.
2. Attempt **ALL** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please write all your answers in the Answer Booklet provided.

Question 1

- (a) Using the Superposition Principle, determine the voltage, v_o in the circuit given in Figure Q1(a).

[11 marks]

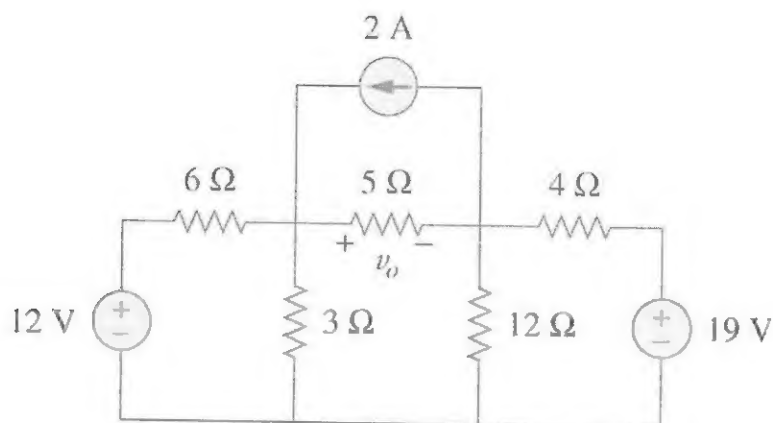


Figure Q1(a)

- (b) Using Norton's Theorem, determine the voltage, V_o in the circuit given in Figure Q1(b).

[14 marks]

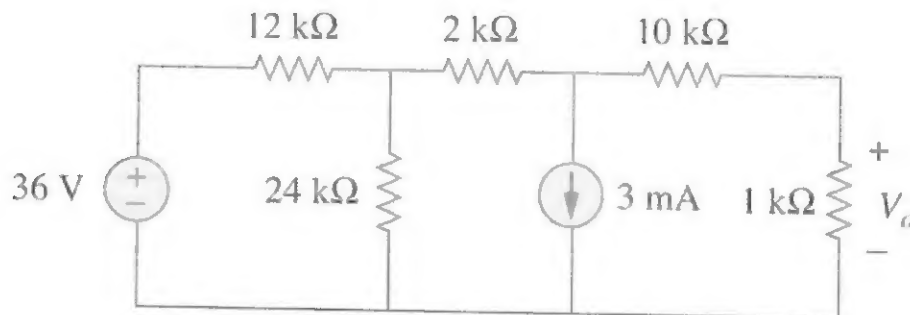


Figure Q1(b).

Continued.....

Question 2

- (a) Define 'Periodic' and 'Aperiodic' signals. Give an example for each.

[3 marks]

- (b) For the waveform shown in Figure Q2(b),

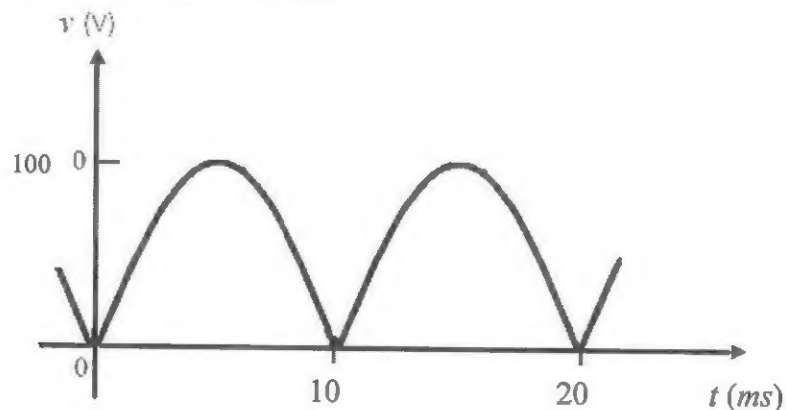


Figure Q2(b)

- (i) calculate the fundamental cyclic frequency, and

[1 mark]

- (ii) find the average value of the waveform.

[5 marks]

- (c) Use the node-voltage method to find the branch currents i_1 , i_2 and i_3 in the circuit of Figure Q2(c). Show that the power developed in the circuit is equal to the power dissipated.

[16 marks]

Continued.....

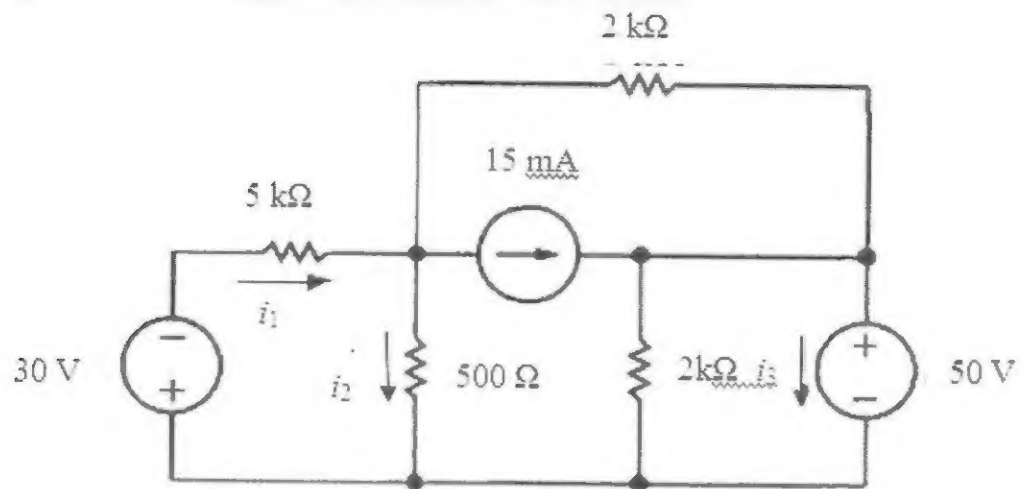


Figure Q2(c)

Question 3

(a) A linear bilateral circuit is shown in Figure Q3(a). Determine the following:

(i) total impedance, Z_T , and

[5 marks]

(ii) total current, I .

[2 marks]

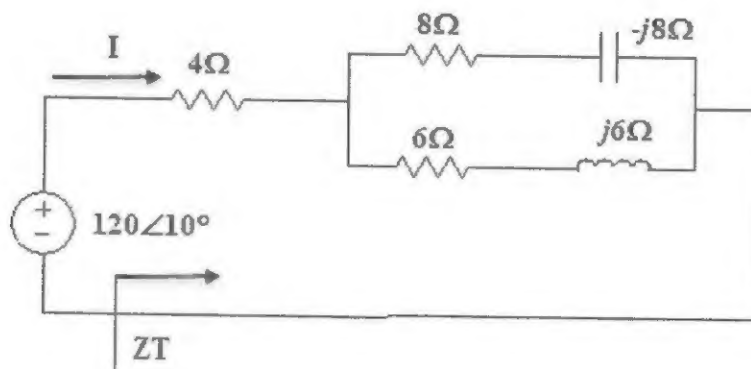


Figure Q3(a)

Continued.....

- (b) The parallel RLC circuit is shown in Figure Q3(b). Determine the following:
- (i) total admittance of the circuit and express the result in polar as well as in rectangular form and also draw admittance diagram, [4 marks]
 - (ii) total impedance of the circuit in polar form, and [2 marks]
 - (iii) total rms current of the circuit. [2 marks]

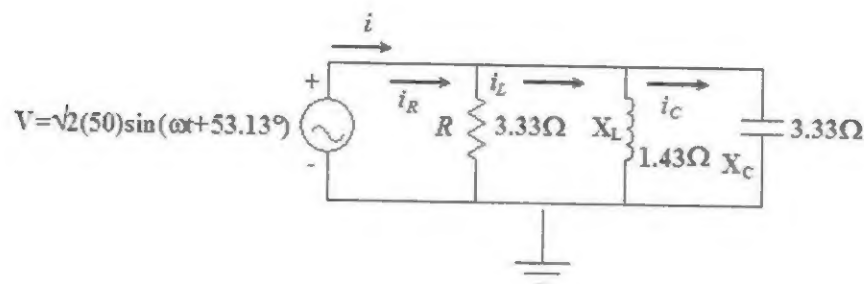


Figure Q3(b)

- (c) A series sinusoidal Steady state RLC circuit is shown in Figure Q3(c). Given values are $R = 20\ \Omega$, $L = 5\text{ mH}$ and $C = 3\text{ pF}$. Determine bandwidth, BW. [10 marks]

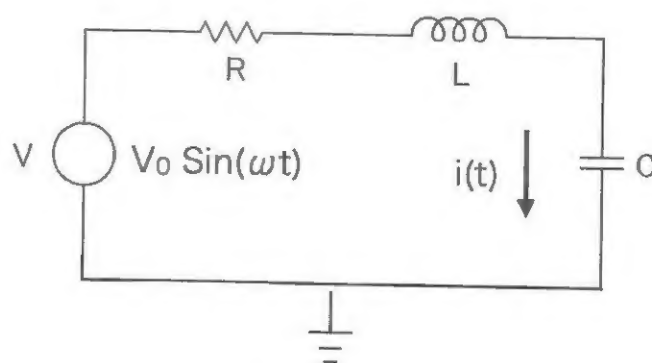


Figure Q3(c)

Continued.....

Question 4

- (a) Determine the capacitor voltage $v(t)$ for $t > 0$ in the circuit of Figure Q4(a). Assume that the switch was open for a long time.

[9 marks]

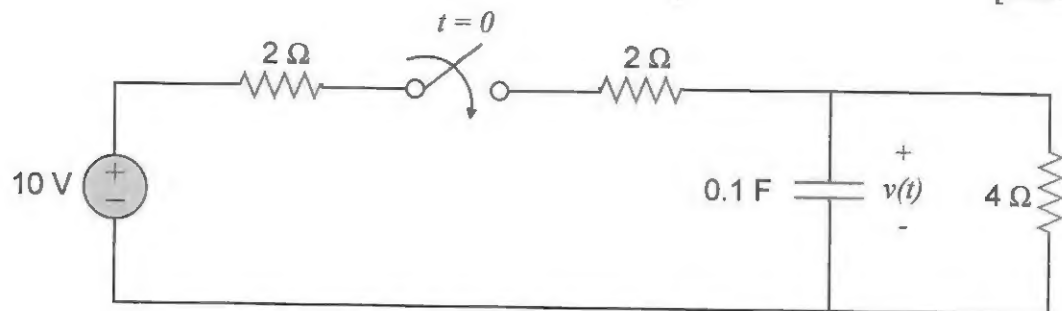


Figure Q4(a)

- (b) The switch in the circuit of Figure Q4(b) has been at position a for a long time. At $t = 0$, it moves to position b . Find $v(t)$ for $t > 0$ in the circuit of Figure Q4(b).

[16 marks]

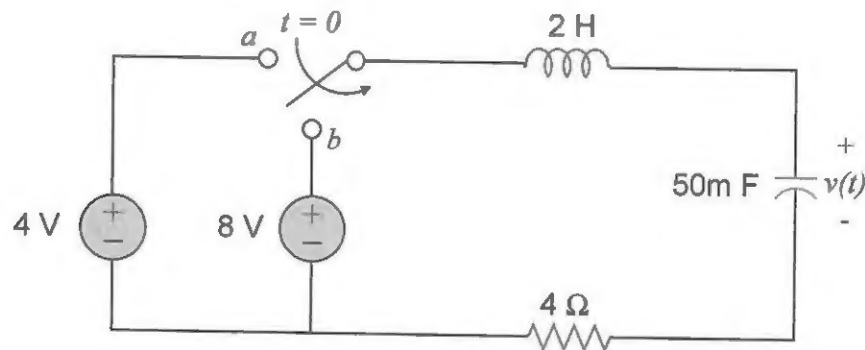


Figure Q4(b)

End of paper